

PASSIVE A/B SWITCHER

There is an inherent problem with most A/B Boxes when running separate effects for each channel. Most A/B Boxes do not ground out the channel not being used, resulting in massive hum + hiss when distortion or fuzz pedals are left on. This design eliminates that problem, and has the purest, non buffered, most transparent tone available.



www.MOUSER.com (800)346-6873
HAMMOND1590B BOX

546-1590B

Yellow LED
Red LED
LED Holder

604-L53YD
604-WP7113HD
606-4304MC


2.1mm DC Jack

171-3215


Switchcraft Mono Jack
Switchcraft Stereo Jack
(only for battery powered)

502-11
502-12B

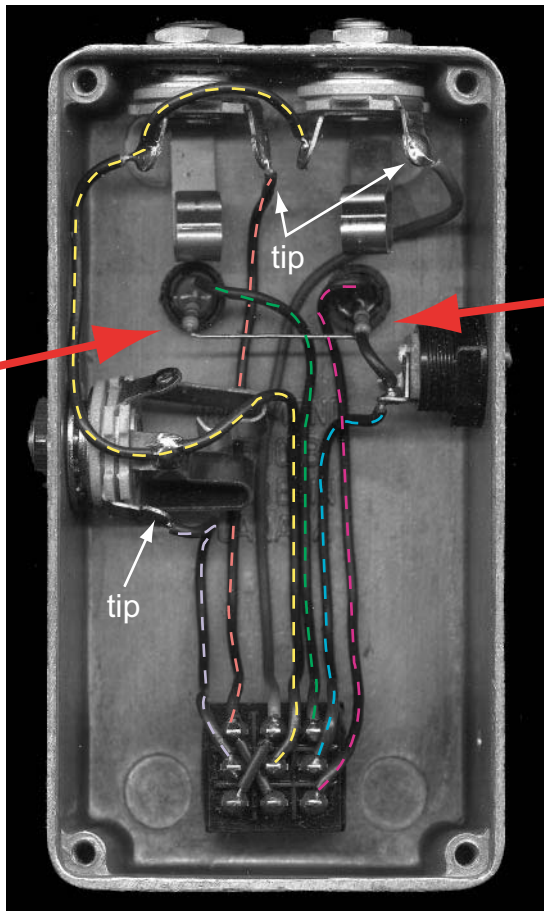3PDT SWITCH (available www.smallbearlelec.com)



2.2K 1/4 watt resistor

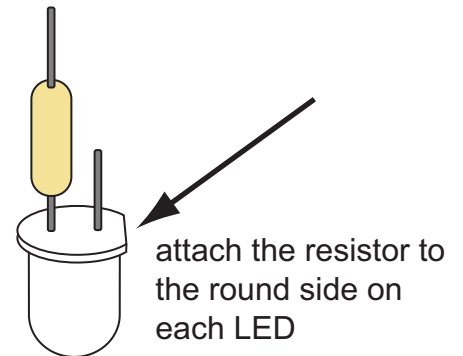

10K 1/4 watt resistor

